

E.D.E.D.C.-IE.D.C.-I

$$\begin{aligned} I_E &= I_B + (\alpha I_E + I_{CBO}) \\ I_B &= I_E - (\alpha I_E + I_{CBO}) \\ I_B &= (1 - \alpha) I_E - I_{CBO} \end{aligned} \quad \dots (5.8)$$

through
in E
dor in t
is la

Neglecting I_{CBO} we can write,

$$I_B = (1 - \alpha) I_E \quad \dots (5.9)$$

Ex. 5.2 : In a certain transistor, 99.6 % of the carriers injected into the base cross the collector-base junction. If the leakage current is $5 \mu A$ and the collector current is $20mA$, calculate (i) the value of α (ii) the emitter current.

Sol.: Given : $I_C = 0.996 I_E$, $I_{CBO} = 5 \mu A$, $I_C = 20 mA$

$$\text{i)} \quad \alpha = \frac{I_C}{I_E} = 0.996$$

$$\text{ii)} \quad \therefore I_E = \frac{I_C - I_{CBO}}{\alpha} = \frac{20 \text{ mA} - 5 \mu \text{A}}{0.996} \\ = 20.07 \text{ mA}$$

From equation

Ex. 5.3 : Calculate the values of collector current and base current for a transistor with α and $I_{CBO} = 10 \mu A$. The emitter current is measured as $8 mA$.

Sol.: Given : $\alpha = 0.99$, $I_{CBO} = 10 \mu A$

From equation

$$\begin{aligned} I_E &= 8 \text{ mA} \\ I_C &= \alpha I_E + I_{CBO} \\ I_C &= 0.99 \times 8 \text{ mA} + 10 \mu \text{A} \\ &= 7.93 \text{ mA} \end{aligned}$$

From equation $I_B = I_E - I_C$

$$\begin{aligned} I_B &= 8 \text{ mA} - 7.93 \text{ mA} \\ &= 70 \mu \text{A} \end{aligned}$$

From equation

5.6.1.2 Common Base

To understand the interrelation of graphically and with most important characteristics.

A) Input Characteristics

It is the curve between (emitter-base voltage taken along Y-axis) and characteristics of a type

From this character

- After the cut-in increase in V_{CB} is small. Because to the resulting (V_{CB}) , this transistor in C

We know that,

Thus

$$\begin{aligned} I_{CBO} &= 5 \mu A \\ I_B &= (1 - \alpha) I_E - I_{CBO} \\ I_E &= \frac{I_B + I_{CBO}}{1 - \alpha} \end{aligned}$$

$$= \frac{100 \mu A + 5 \mu A}{1 - 0.98}$$

$$= \frac{105 \mu A}{0.02} = 5.25 \text{ mA}$$

From equation $I_C = I_E - I_B$ we get,

$$I_C = 5.25 \text{ mA} - 100 \mu A = 5.15 \text{ mA}$$

Ex. 5.5 : For a certain transistor, $\alpha = 0.98$, $I_C = 5 \text{ mA}$ and $I_{CBO} = 10 \mu A$. Find I_B .

Sol. : Given $I_C = 5 \text{ mA}$

$$I_{CBO} = 10 \mu A$$

$$\alpha = 0.98$$

We know that,

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = \frac{I_C - I_{CBO}}{\alpha}$$

$$= \frac{5 \text{ mA} - 10 \mu A}{0.98}$$

$$= 5.092 \text{ mA}$$

From equation $I_B = I_E - I_C$ we get,

$$I_B = 5.092 \times 10^{-3} - 5 \times 10^{-3} = 92 \mu A$$

5.6.1.2 Common Base Characteristics

To understand complete electrical behaviour of a transistor it is necessary to study the interrelation of the various currents and voltages. These relationships can be plotted graphically and which are commonly known as the **characteristics of transistor**. The most important characteristics of transistor in any configuration are input and output characteristics.

A) Input Characteristics :

It is the curve between input current I_E (emitter current) and input voltage V_{EB} (emitter-base voltage) at constant collector-base voltage V_{CB} . The emitter current is taken along Y-axis and emitter base voltage along X-axis. Fig. 5.16 shows the input characteristics of a typical transistor in common-base configuration.

From this characteristics we can observe the following important points :

- After the cut-in voltage, the emitter current (I_E) increases rapidly with small increase in emitter-base voltage (V_{EB}). It means that input resistance is very small. Because input resistance is a ratio of change in emitter-base voltage (ΔV_{EB}) to the resulting change in emitter current (ΔI_E) at constant collector-base voltage (V_{CB}), this resistance is also known as the **dynamic input resistance** of the transistor in CB configuration.

E

E.D.C.-I

Substituting the value of I_B in equation (5.14) we get,

$$\beta = \frac{I_C}{I_E - I_C}$$

E.D.C.-I

Dividing the numerator and denominator of R.H.S. of equation (5.16) by I_E , we get

$$\beta = \frac{\frac{I_C}{I_E}}{\frac{I_E - I_C}{I_E}}$$

b)

We know that, $\alpha = \frac{I_C}{I_E}$ from equation (5.15)

$$\beta = \frac{\alpha}{1 - \alpha}$$

Ex. 5.7 : If the base current is 100 μA , find the value of β .

Sol.: Given : $I_B = 100 \mu A$

b) Dividing the R.H.S. and L.H.S. by $1 + \beta$ we get,

$$\frac{\beta}{1 + \beta} = \frac{\alpha}{1 - \alpha}$$

By substituting value of β from equation (5.17) in R.H.S. we get,

$$\frac{\beta}{1 + \beta} = \frac{\frac{\alpha}{1 - \alpha}}{1 + \frac{\alpha}{1 - \alpha}}$$

$$\frac{\beta}{1 + \beta} = \frac{\frac{\alpha}{1 - \alpha}}{\frac{1 - \alpha + \alpha}{1 - \alpha}}$$

Cancelling common denominator terms we get,

$$\frac{\beta}{1 + \beta} = \frac{\alpha}{1 - \alpha + \alpha} = \alpha$$

$$\alpha = \frac{\beta}{1 + \beta}$$

Ex. 5.6 : a) Find α for each of the following values of $\beta = 50$ and 190
 b) Find β for each of the following values of $\alpha = 0.995$ and 0.9765

Sol. : a)

$$\alpha = \frac{\beta}{\beta + 1}$$

Ex. 5.8 : In a certain transistor, $\alpha = 0.995$. Calculate the collector-base voltage if the collector current is 100 μA .

Sol. : Given : $I_C = 100 \mu A$

i)

$$\beta = 50, \quad \alpha = \frac{50}{50 + 1} = 0.9804$$

$$\beta = 190, \quad \alpha = \frac{190}{190 + 1} = 0.9947$$

b) $\beta = \frac{\alpha}{1 - \alpha}$

$$\alpha = 0.995, \quad \beta = \frac{0.995}{1 - 0.995} = 199$$

$$\alpha = 0.9765, \quad \beta = \frac{0.9765}{1 - 0.9765} = 41.55$$

Ex. 5.7 : If the base current in a transistor is $20 \mu\text{A}$ when the emitter current is 6.4 mA , what are the values of α and β ? Also calculate the collector current.

Sol.: Given : $I_B = 20 \mu\text{A}$ $I_E = 6.4 \text{ mA}$

$$\begin{aligned} I_C &= I_E - I_B \\ &= 6.4 \text{ mA} - 20 \mu\text{A} \\ &= 6.38 \text{ mA} \\ \therefore \quad \beta &= \frac{I_C}{I_B} = \frac{6.38 \text{ mA}}{20 \mu\text{A}} \\ &= 319 \\ \alpha &= \frac{\beta}{\beta + 1} = \frac{319}{319 + 1} \\ &= 0.9968 \end{aligned}$$

Ex. 5.8 : In a certain transistor, 99.6% of the carriers injected into the base cross the collector-base junction. If the leakage current is $5 \mu\text{A}$ and the collector current is 20 mA , calculate (i) the value of α (ii) the emitter current.

Sol.: Given : $I_C = 0.996 I_E$, $I_{CBO} = 5 \mu\text{A}$, $I_C = 20 \text{ mA}$

i) $\alpha = \frac{I_C}{I_E} = 0.996$

$$\begin{aligned} I_C &= \alpha I_E + I_{CBO} \\ \therefore \quad I_E &= \frac{I_C - I_{CBO}}{\alpha} \\ &= \frac{20 \text{ mA} - 5 \mu\text{A}}{0.996} \\ &= 20.07 \text{ mA} \end{aligned}$$

E.D.C.-I

Ex. 5.9: The reverse leakage current of the transistor, when connected in common-base configuration is $0.1 \mu\text{A}$, while it is $16 \mu\text{A}$ when the same transistor is connected in common-emitter configuration. Calculate the α and β of the transistor.

Sol.: Given: $I_{CBO} = 0.1 \mu\text{A}$, $I_{CEO} = 16 \mu\text{A}$

$$I_{CEO} = \frac{1}{1 - \alpha} I_{CBO}$$

$$1 - \alpha = \frac{I_{CBO}}{I_{CEO}}$$

$$\alpha = 1 - \frac{I_{CBO}}{I_{CEO}} = 0.993$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.993}{1 - 0.993} = 159$$

5.6.2.3 Common Emitter Characteristics**A) Input Characteristics :**

It is the curve between input current I_B (base current) and input voltage V_{BE} (base-emitter voltage) at constant collector-emitter voltage, V_{CE} . The base current is taken along Y-axis and base emitter voltage V_{BE} is taken along X-axis. Fig. 5.27 shows the input characteristics of a typical transistor in common-emitter configuration.

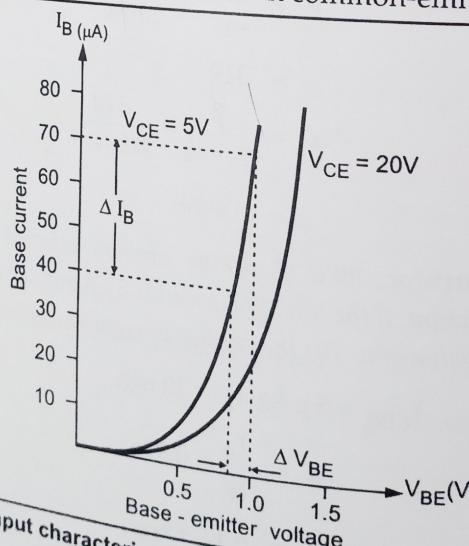


Fig. 5.27 Input characteristics of the transistor in CE configuration

From this characteristics we observe the following important points :

- As the input to a transistor in the CE configuration is between the base-to-emitter junction, the CE input characteristics resembles a family of forward-biased diode curves. A typical set of CE input characteristics for an n-p-n transistor is shown in Fig. 5.27.

E.D.C.-I

- After increasing small to the V_{CE} . It

- For a fixed results depletion fewer re

B) Output Characteristics

- This characteristic called collector current of n-p-n transistors

Saturation region

Fig. 5.28

- The value of β taking the ratio of I_C to I_B for the transistor